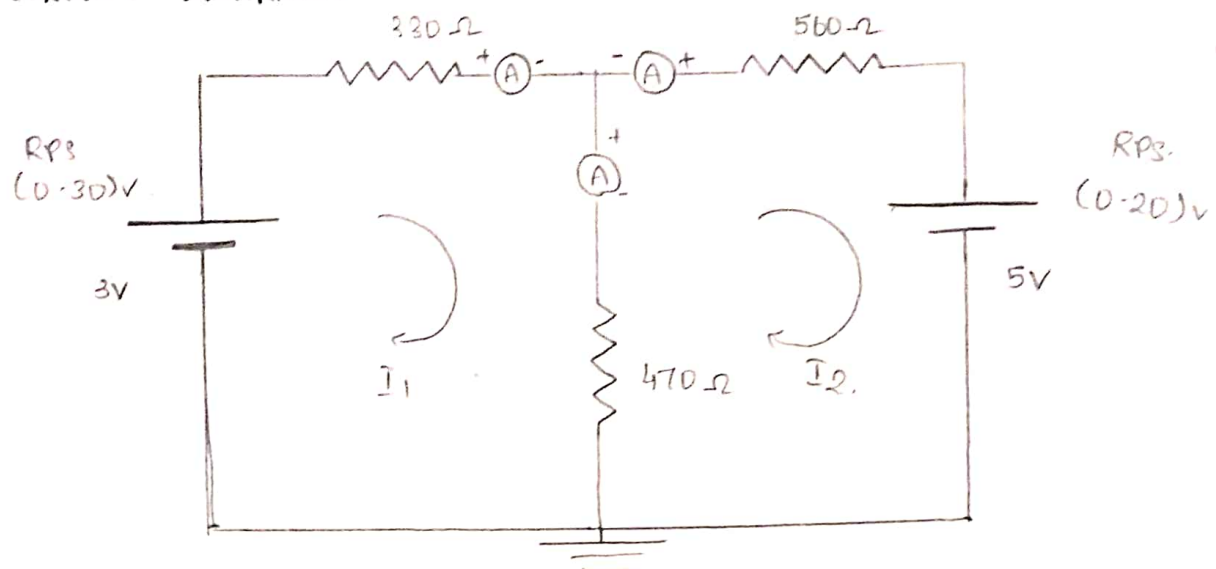


CIRCUIT DIAGRAM:-



TABULAR COLUMN:-

Parameters	Theoretical	Practical
I_1	$0.0090 A$	$0.089 A$
I_2	$0.0089 A$	$0.076 A$
$I_1 - I_2$	$0.00012 A$	$0.0012 A$

Loop 1:

$$-3 + 330 I_1 + 470 (I_1 - I_2) = 0$$

$$800 I_1 - 470 I_2 = 3 \longrightarrow \textcircled{1}$$

Loop 2:

$$-5 + 560 I_2 + 470 (I_2 - I_1) = 0$$

$$-470 I_1 + 1030 I_2 = 5 \longrightarrow \textcircled{2}$$

DETERMINATION OF CURRENT IN CIRCUIT USING MESH ANALYSIS.

AIM:

To determine the current in circuit using mesh analysis both theoretically and practically for a given DC circuit.

APPARATUS REQUIRED:

S.No	APPARATUS	SPECIFICATION	QUANTITY
1.	Regulated Power supply (RPS)	(0-30V)	1
2.	Ammeter.	(0-10mA) MC	3
3.	Resistors	330 Ω , 470 Ω , 560 Ω	each 1.
4.	Bread board	-	1

PROCEDURE:

1. Give connections as per the circuit diagram.
2. Switch on the supply, vary the RPS and set a particular input voltage.
3. Note down the readings of ammeters and voltmeters and tabulate them.
4. Vary the RPS for different input voltages and note down the readings of all the meters.
5. Reduce the RPS to its minimum value and switch off the supply.

$$103 \times 10^{-3} \rightarrow 82400 I_1 - 48410 I_2 = 309$$

$$-22090 I_1 + 48410 I_2 = 235$$

$$\hline 60310 I_1 = 544$$

$$I_1 = \frac{544}{60310}$$

$$= 9.02 \times 10^{-3}$$

Sub eq I_1 in equation ①,

$$800 [0.009] - 470 I_2 = 3$$

$$7.2 - 470 I_2 = 3$$

$$-470 I_2 = 3 - 7.2$$

$$-470 I_2 = -4.2$$

$$I_2 = \frac{4.2}{470} = 0.0089$$

$$I_2 = 8.97 \text{ mA}$$

$$I_1 - I_2 = 9.02 - 8.97$$

$$= 0.05 \text{ mA}$$

6. Using the tabulated values, verify Kirchhoff's laws practically and verify it theoretically.

RESULT:

Thus the mesh analysis is verified practically and theoretically the resultant currents for 5V 3V supply are,

a) The current across 330Ω resistor is 0.0090

b) The current across 560Ω resistor is 0.0089 .

c) The current across 470Ω resistor is 0.00012 .